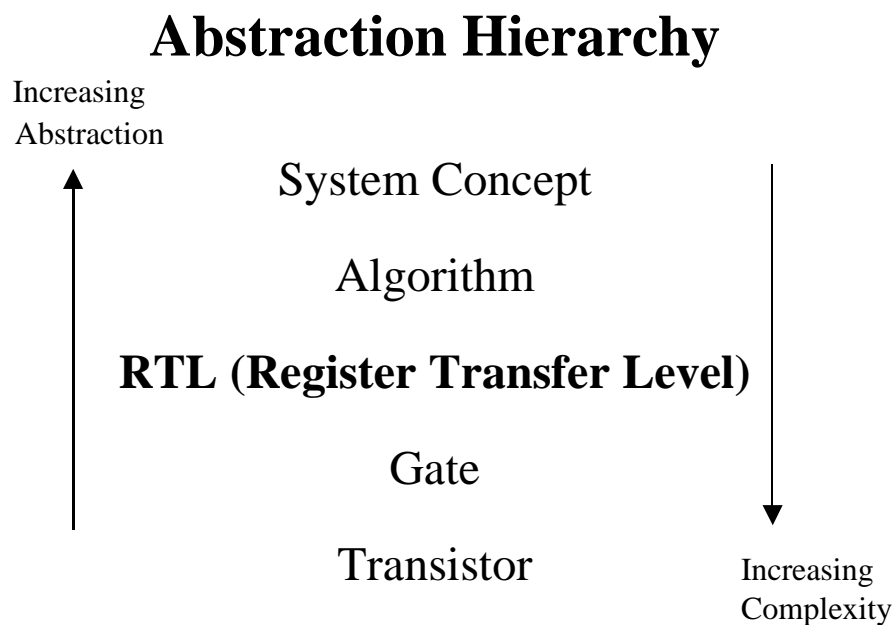


What is VHDL?

- A *hardware description language* that can be used to model a digital system.
- VHDL = VHSIC Hardware Description Language
- Very High Speed Integrated Circuit
- Can describe:
 - behaviour,
 - structure, and
 - timingof a logic circuit.

Hardware Modelling in VHDL

- VHDL is **NOT** a programming language like C or Java.
- It is used to model the physical hardware used in digital systems.
- Therefore you must always think about the hardware you wish to implement when designing systems using VHDL.



Data Objects

- A *data object* holds a value of a specified type.
- The data objects that can be synthesized directly in hardware are:
 1. **Signal:** Represents a physical wire in a circuit. It holds a list of values which includes its current value and a set of possible future values.
 2. **Variable:** Used to hold results of computations. It does not necessarily represent a wire in a circuit.
 3. **Constant:** Contains a value that cannot be changed. It is set before the beginning of a simulation.

Predefined Data Types

- Standard logic type: STD_LOGIC,
 STD_LOGIC_VECTOR
 (Can hold 0, 1, Z, and --.)
- Bit type: BIT, BIT_VECTOR
- Integer type: INTEGER
- Floating–point type: REAL
- Physical type: TIME
- Enumeration type: BOOLEAN, CHARACTER

- To use the STD_LOGIC and
STD_LOGIC_VECTOR types, the *std_logic_1164*
package must be included in the VHDL design file.

- We can define our own data types. This is
especially useful when designing finite–state machines
(FSMs).

- An object declaration is used to declare an object, its
type, its class, and optionally to assign it a value.

Object Declaration Examples

- Signal declarations:
SIGNAL sresetn : STD_LOGIC;
SIGNAL address : STD_LOGIC_VECTOR(7
downto 0);
- Variable declarations:
VARIABLE index : INTEGER range 0 to 99 :=
20;
VARIABLE memory : BIT_MATRIX(0 to 7, 0
to 1023);
- Constant declarations:
CONSTANT cycle_time : TIME := 100 ns;
CONSTANT cst : UNSIGNED(3 downto 0);

Operators

	Operator Class	Operator
Highest Precedence	Miscellaneous	** , ABS , NOT
	Multiplication	* , / , MOD , REM
	Unary Arithmetic (Sign)	+ , -
	Addition	+ , - , &
	Shift/Rotate	sll , srl , sla , sra , rol , ror
	Lowest Precedence	Relational
Logical		and , or , nand , nor , xor , xnor

- The individual operators in each class have the same precedence.

VHDL Design Entity

Design Entity

Entity Declaration

- Specifies the interface of entity to the outside world.
- Has a name.
- Includes PORT statement which specifies the entity's input and output signals (ports)
 - Ports can have different modes:
 - IN
 - OUT
 - INOUT
 - BUFFER

Architecture


- Provides circuit details for an entity
 - General form:

```
ARCHITECTURE arch_name OF entity_name IS
    Signal declarations
    Constant declarations
    Type declarations
    Component declarations
BEGIN
    Component instantiations
    Concurrent assignment statements
    Process statements
END arch_name
```

Concurrent Assignment Statements

- A concurrent assignment statement is used to assign a value to a signal in an architecture body.
- Used to model combinational circuits.
- The order in which these statements occur does not affect the meaning of the code.


2x4 Decoder Example

 

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
```

```
ENTITY decoder2x4 IS
    PORT (A, B, EN : IN STD_LOGIC;
          Z : OUT STD_LOGIC_VECTOR(3 downto 0));
END decoder2x4;
--this is a comment
```

Architecture Body of 2x4 Decoder

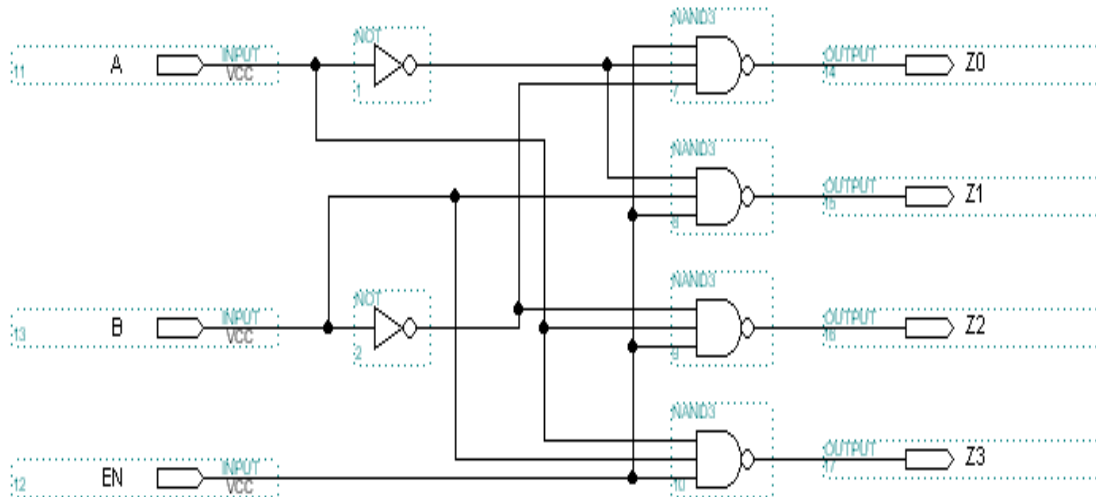

```
ARCHITECTURE dec_df OF decoder2x4 IS
    SIGNAL ABAR, BBAR : STD_LOGIC;
BEGIN
    --Order of concurrent signal assignment
    statements is not important.
    Z(3) <= not (A and B and EN);
    Z(0) <= not (ABAR and BBAR and EN);
    BBAR <= not B;
    Z(2) <= not (A and BBAR and EN);
    ABAR <= not A;
    Z(1) <= not (ABAR and B and EN);
END dec_df;
```

Sequential Assignment Statements

- Sequential assignment statements assign values to signals and variables. The order in which these statements appear can affect the meaning of the code.
- Can be used to model combinational circuits and sequential circuits.
- Require use of the PROCESS statement.
- Include three variants: IF statements, CASE statements, and LOOP statements.

2x4 Decoder Revisited

```
ARCHITECTURE dec_seq OF decoder2x4 IS
BEGIN
    PROCESS(A, B, EN) --Sensitivity list
        VARIABLE ABAR, BBAR : STD_LOGIC;
    BEGIN
        --Variable values assigned immediately.
        ABAR := not A;
        BBAR := not B;
        IF (EN = '1') THEN
            Z(3) <= not(A and B);
            Z(2) <= not(A and BBAR);
            Z(1) <= not(ABAR and B);
            Z(0) <= not(ABAR and BBAR);
        ELSE
            Z <= "1111";
        END IF;
    END PROCESS;
END dec_seq;
```

IF and CASE Statements

- IF and CASE statements are used to model multiplexers, decoders, encoders, and comparators.
- Can only be used in a PROCESS.

Modelling a 4–1 Multiplexer

Using an IF statement:


```
PROCESS (Sel, A, B, C, D)
BEGIN
    IF (Sel = "00") THEN
        Y <= A;
    ELSIF (Sel = "01")
    THEN
        Y <= B;
    ELSIF (Sel = "10")
    THEN
        Y <= C;
    ELSE
        Y <= D;
    END IF;
END PROCESS;
```

Using a CASE statement:

```
PROCESS (Sel, A, B, C, D)
BEGIN
    CASE Sel IS
        WHEN "00" => Y <= A;
        WHEN "01" => Y <= B;
        WHEN "10" => Y <= C;
        WHEN "11" => Y <= D;
        WHEN OTHERS => Y
        <=A;
    END CASE;
END PROCESS;
```

- Can also model multiplexers with WHEN/ELSE clause and WITH/SELECT clause. These can only be used outside of a PROCESS.

FSM Example

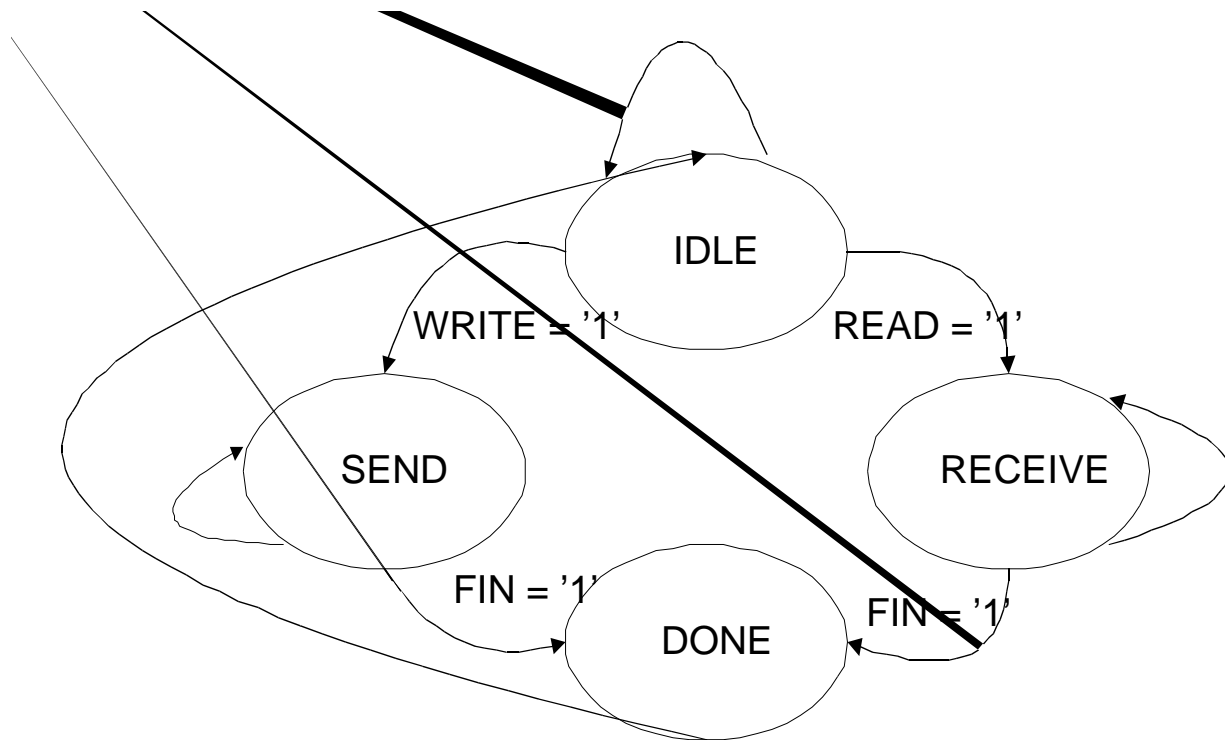


```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY Controller IS
```

```
    PORT ( Write, Read, Fin      : IN STD_LOGIC;  
          Busy, Snd, Rec, Dn    : OUT STD_LOGIC;  
          Clock                  : IN STD_LOGIC;  
          Reset                  : IN STD_LOGIC);
```

```
END Controller;
```


FSM Example Continued

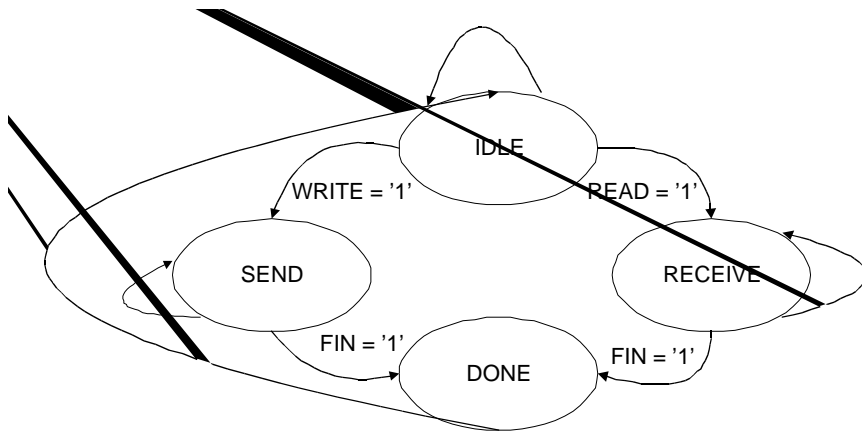

```
ARCHITECTURE My_FSM OF Controller IS
  TYPE State_Type IS (Idle, Send, Receive,
                      Done);
  SIGNAL State : State_Type;
```

```
BEGIN
  PROCESS(Reset, Clock)
  BEGIN
    IF Reset='1' THEN
      State <= Idle;
    ELSIF(Clock'EVENT and Clock='1') THEN
      CASE State IS
        WHEN Idle =>
          IF Read='1' THEN
            State <= Receive;
          ELSIF Write='1' THEN
            State <= Send;
          ELSE
            State <= Idle;
          END IF;
        END CASE;
      END IF;
```

FSM Example Continued

 

```
WHEN Receive =>
  IF Fin='1' THEN
    State <= Done;
  END IF;
```

```
WHEN Send =>
  IF Fin='1' THEN
    State <= Done;
  END IF;
```

```
WHEN Done =>
  State <= Idle;
END CASE;
END IF;
END PROCESS;
```


```
Busy <= '0' WHEN State = Idle ELSE '1';
Rec <= '1' WHEN State = Receive ELSE '0';
Snd <= '1' WHEN State = Send ELSE '0';
Dn <= '1' WHEN State = Done ELSE '0';
```

```
END My_FSM;
```


Behavioural vs. Structural Modelling

- With VHDL, we can describe the behaviour of simple circuit building blocks and then use these to build up the structure of a more complex circuit.
- Behavioural modelling is useful because it allows the designer to build a logic circuit without having to worry about the low-level details.
- Structural modelling is useful because it tells the synthesis tools exactly how to construct a desired circuit.

Behavioural Model of a D Flip-Flop

 

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY my_dff IS
    PORT ( D : IN  STD_LOGIC;
          Q : OUT STD_LOGIC;
          Clock : IN  STD_LOGIC;
          Resetn: IN  STD_LOGIC);
END my_dff;

ARCHITECTURE Behaviour OF my_dff IS
BEGIN
    PROCESS(Clock, Resetn)
    BEGIN
        IF Resetn='0' THEN
            Q <= '0';
        ELSIF (Clock'EVENT AND Clock='1') THEN
            Q <= D;
        END IF;
    END PROCESS;
END Behaviour;
```

Behavioural Model of a 4–Bit Shift Register

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY shift_reg_behav IS
    PORT ( Data_IN : IN STD_LOGIC;
          Data_OUT : OUT STD_LOGIC;
          Clock, Resetn : IN STD_LOGIC);
END shift_reg_behav;

ARCHITECTURE Behaviour OF shift_reg_behav IS
    SIGNAL Shift : STD_LOGIC_VECTOR(3 downto
    0);
BEGIN
    PROCESS(Clock, Resetn)
    BEGIN
        IF Resetn='0' THEN
            Shift <= "0000";
        ELSIF (Clock'EVENT AND Clock='1') THEN
            Shift(3) <= Data_IN;
            --shift data to the right
            Shift(2 downto 0) <= Shift(3 downto 1);
        END IF;
    END PROCESS;

    Data_OUT <= Shift(0);

END Behaviour;
```

 
Structural Model of a 4–Bit Shift Register



```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;
```

```
ENTITY shift_reg_struct IS  
    PORT (Data_IN : IN STD_LOGIC;  
          Data_OUT: OUT STD_LOGIC;  
          CLK, RESN : IN STD_LOGIC);  
END shift_reg_struct;
```

 Structural Model of a 4–Bit Shift Register Cont.



ARCHITECTURE Structure OF shift_reg_struct IS

COMPONENT my_dff

```
PORT ( D : IN STD_LOGIC;  
       Q : OUT STD_LOGIC;  
       Clock : IN STD_LOGIC;  
       Resetn: IN STD_LOGIC);
```

END COMPONENT;

```
SIGNAL Q3_out, Q2_out, Q1_out : STD_LOGIC;
```

BEGIN

```
DFF_3 : my_dff PORT MAP (Data_IN, Q3_out, CLK, RESN);
```

```
DFF_2 : my_dff PORT MAP (Q3_out, Q2_out, CLK, RESN);
```

```
DFF_1 : my_dff PORT MAP (D=>Q2_out, Q=>Q1_out,  
                        Clock=>CLK, Resetn=>RESN);
```

```
DFF_0 : my_dff PORT MAP (D=>Q1_out, Q=>Data_OUT,  
                        Clock=>CLK, Resetn=>RESN);
```

END Structure;

Using Altera's Library of Parameterized Modules (LPMs)

- Altera MAX+plus II has numerous predefined circuit building blocks in its LPMs.
- These libraries include everything from full-adders to ROMs.

Altera LPM Flip-Flop

- Must include library and use:

```
LIBRARY lpm;
```

```
USE lpm.lpm_components.all;
```

```
COMPONENT lpm_ff
```

```
  GENERIC (LPM_WIDTH: POSITIVE;
```

```
    LPM_AVALUE: STRING := "UNUSED";
```

```
    LPM_FFTYPE: STRING := "FFTYPE_DFF";
```

```
    LPM_TYPE: STRING := "L_FF";
```

```
    LPM_SVALUE: STRING := "UNUSED";
```

```
    LPM_HINT: STRING := "UNUSED");
```

```
  PORT (data: IN STD_LOGIC_VECTOR(LPM_WIDTH-1  
    DOWNTO 0);
```

```
    clock: IN STD_LOGIC;
```

```
    enable: IN STD_LOGIC := '1';
```

```
    sload: IN STD_LOGIC := '0';
```

```
    sclr: IN STD_LOGIC := '0';
```

```
    sset: IN STD_LOGIC := '0';
```

```
    aload: IN STD_LOGIC := '0';
```

```
    aclr: IN STD_LOGIC := '0';
```

```
    aset: IN STD_LOGIC := '0';
```

```
    q: OUT STD_LOGIC_VECTOR(LPM_WIDTH-1 DOWNTO  
    0));
```

```
END COMPONENT;
```

Altera LPM Flip–Flop Device Description

Ports:

INPUTS

Port Name	Required	Description	Comments
data[]	No	T-type flipflop: Toggle enable D-type flipflop: Data input	Input port LPM_WIDTH wide. If the data[] input is not used, at least one of the aset, aclr, sset, or sclr ports must be used. Unused data inputs default to GND.
clock	Yes	Positive-edge-triggered Clock.	
enable	No	Clock Enable input.	Default = 1.
sclr	No	Synchronous Clear input.	If both sset and sclr are used and both are asserted, sclr is dominant. The sclr signal affects the output q[] values before polarity is applied to the ports.
sset	No	Synchronous set input.	Sets q outputs to the value specified by LPM_SVALUE, if that value is present, or sets the q outputs to all 1's. If both sset


OUTPUTS

Port Name	Required	Description	Comments
q[]	Yes	Data output from D or T flipflops.	Output port LPM_WIDTH wide.

Parameters:

Parameter	Type	Required	Description
LPM_WIDTH	Integer	Yes	Width of the data[] and q[] ports.
LPM_AVALUE	Integer	No	Constant value that is loaded when aset is high. If omitted, defaults to all 1's. The LPM_AVALUE parameter is limited to a maximum of 32 bits.
LPM_SVALUE	Integer	No	Constant value that is loaded on the rising edge of clock when sset is high. If omitted, defaults to all 1's.
LPM_FFTYPE	String	No	Values are "DFF", "TFF", and "UNUSED". Type of flipflop. If omitted, the default is "DFF". When the LPM_FFTYPE parameter is set to "DFF", the sload port is ignored.
LPM_HINT	String	No	Allows you to specify Altera-specific parameters in VHDL Design Files. The default is "UNUSED".
LPM_TYPE	String	No	Identifies the LPM entity name in VHDL Design Files.

 Structural Description of Shift Register Using Altera's Flip-Flop LPM



```
LIBRARY ieee;  
USE ieee.std_logic_1164.all;  
LIBRARY lpm;  
USE lpm.lpm_components.all;
```

```
ENTITY shift_reg_struct2 IS
```

```
PORT (
```

```
    Data_IN : IN STD_LOGIC_VECTOR(0 downto 0);
```

```
    Data_OUT: OUT STD_LOGIC_VECTOR(0  
        downto 0);
```

```
    CLK, RESN : IN STD_LOGIC);
```

```
END shift_reg_struct2;
```


Structural Description of Shift Register Using Altera's Flip-Flop LPM Cont.

```
ARCHITECTURE Structure OF shift_reg_struct2 IS
    SIGNAL Q3_out, Q2_out, Q1_out :
        STD_LOGIC_VECTOR(0 downto 0);
    SIGNAL Reset_Internal : STD_LOGIC;

BEGIN
    Reset_Internal <= not RESN;

    DFF_3 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
        LPM_FFTYPE=>"DFF")
        PORT MAP (data=>Data_IN, q=>Q3_out,
            clock=>CLK, aclr=>Reset_Internal);

    DFF_2 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
        LPM_FFTYPE=>"DFF")
        PORT MAP (data=>Q3_out, q=>Q2_out,
            clock=>CLK, aclr=>Reset_Internal);

    DFF_1 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
        LPM_FFTYPE=>"DFF")
        PORT MAP (data=>Q2_out, q=>Q1_out,
            clock=>CLK, aclr=>Reset_Internal);

    DFF_0 : lpm_ff GENERIC MAP (LPM_WIDTH=>1,
        LPM_FFTYPE=>"DFF")
        PORT MAP (data=>Q1_out, q=>Data_OUT,
            clock=>CLK, aclr=>Reset_Internal);

END Structure;
```